

Rajshahi University of Engineering & Technology
Department of Electrical and Electronic Engineering

Course No.: EEE 1203

Course Title: Electronics I

Course Teachers: Dr. Abdul Khaleque

Section: A & B; Marks: 20

Assignment-01

No.	Question / Problem	Marks
01	Design a series diode circuit having a dc supply, one Si diode, one Ge diode and one resistor (load), hence, calculate the current passing through the load. The value of the load is last three digit of your roll number (in $k\Omega$).	04
02	Design a diode circuit having a dc supply, one Si diode, one Ge diode and one resistor (load). Two diodes as well as load are connected in parallel. Calculate the current passing through each parallel branch. The value of the load is last three digit of your roll number (in $k\Omega$).	04
03	Design a diode circuit having series parallel configurations with a dc supply, diodes and one resistor (load). Calculate the current passing through the required branches. The value of the load is last two digit of your roll number (in $k\Omega$).	04
04	Design a positive logic AND gate operation by using two Si diodes and a load. The value of the load is last two digit of your roll number (in $k\Omega$).	04
05	A full-wave bridge rectifier with a 120-V rms sinusoidal input has a load resistor of last two digit of your roll number (in $k\Omega$). (a) If silicon diodes are employed, what is the dc voltage available at the load? (b) Determine the required PIV rating of each diode. (c) Find the maximum current through each diode during conduction. (d) What is the required power rating of each diode?	04

Please write your roll number carefully in the answer sheet. Last date and time of submission through class representative (CR): Coming Saturday within 10:30 AM.

Heaven's Light is Our Guide



Rajshahi University of Engineering & Technology

Dept. of Electrical and Electronic Engineering

ASSIGNMENT-01

Course Title: Electronics I

Course Code: EEE 1203

Submitted By :	Submitted To :
Name : Mir Masrur Roll : 2001019 Section : A Date :	Dr. Abdul Khaleque Professor Dept. of Electrical and Electronic Engineering, RUET









